

# Digital Electronic

BScv 2016 - 2017  
2<sup>nd</sup> semester

Cédric Lemaître  
c.lemaitre58@gmail.com

*Université de Bourgogne*



# 1 Digital Electronic Basics

## Considering a real problem



## Digital Electronics Basics

### Considering a real problem

#### Problem

A tank is filled by 2 pipes :  $V_1$  and  $V_2$ . We consider 3 levels

- ▶ Warning (W)
- ▶ Bottom (B)
- ▶ top (T)

When level is behind W,  $V_1$  et  $V_2$  are opened.

When level is between W and B, only  $V_1$  is opened.

When level is between B and T, only  $V_2$  is opened.

When level is upper T, we close the pipe.



## Digital Electronics Basics

### Considering a real problem

How to do?

- ▶ Make a drawing



## Digital Electronics Basics

### Considering a real problem

#### How to do?

- ▶ Make a drawing
- ▶ Make the truth table



## Digital Electronics Basics

### Considering a real problem

#### How to do?

- ▶ Make a drawing
- ▶ Make the truth table
- ▶ Reduce complexity by using Karnaugh table and rules



## Digital Electronics Basics

### Considering a real problem

#### Implementation using Electronic component

- Which Family? CMOS or TTL technology?



Figure: TTL 7406



## Digital Electronics Basics

### Techno - information

#### TTL

- ▶ Input voltage 5V  $\pm 5\%$
- ▶ 0 : 0.4V–0.8V
- ▶ 1 : 2.4V–2.8V
- ▶ TP : 10ns for "N" series  
and 1.5ns for "AS"

#### CMOS


- ▶ Input voltage 3 to 18V
- ▶ 0 :  $0.05V_{cc}$ – $0.45V_{cc}$
- ▶ 1 :  $0.55V_{cc}$ – $0.95V_{cc}$
- ▶ TP : depending of  $V_{cc}$





# Digital Electronics Basics

## Techno - information

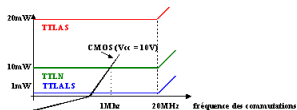



## Digital Electronics Basics

### Considering a real problem

#### Implementation using Electronic component

- ▶ Which Family? CMOS or TTL technology?
- ▶ Find components you need and corresponding datasheet



Figure: TTL 7406



## Digital Electronics Basics

### Considering a real problem

#### Implementation using Electronic component

- ▶ Which Family? CMOS or TTL technology?
- ▶ Find components you need and corresponding datasheet
- ▶ Make the wiring of the circuit



Figure: TTL 7406